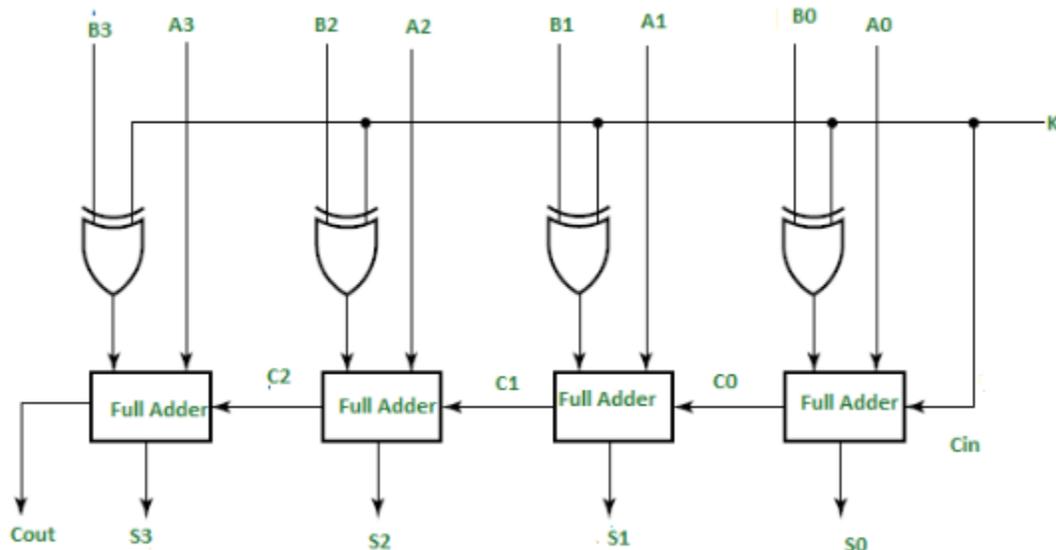




<p>Course: Digital Engineering</p> <p>Semester: 1st term 2025/2026.</p>	<p>Lecturers: Dr. Osama Elnahas, Dr. Dina Abdelhafiz, Dr. Bassant Tolba, Dr. Radwa Rady</p> <p>Assistant: Eng. Rania Helal, Eng. Assma, Eng. Israa Mohsen, Eng. Ahmed Kamel, Eng. Belal,</p>
<p>DE ASSIGNMENT 4</p>	

Question 1: Full Adder and Subtraction



There is a control line K (M in your slides) that holds a binary value of either 0 or 1 which determines that the operation is carried out is addition or subtraction.

M = 0 → Perform A + B

M = 1 → Perform A – B using 2’s complement

Assume that we have two 3-bit numbers and feed them in Full-Adder as an input. Find the output sum (s3,s2,s1,s0) and cout for the following:

- M=0 , A=100 , B=011
- M=1 , A=100, B=011
- M=0 , A=111 , B=111
- M=1 , A=111 , B=111
- M=0 , A=101 , B=101
- M=1 , A=101 , B=101

Question 2:

1. A Half Adder adds two:
A) 3-bit numbers B) 2 single bits C) Signed bits D) Hex values
2. The sum output of a Half Adder is given by:
A) $A \cdot B$ B) $A + B$ C) $A \oplus B$ D) $A \odot B$
3. The carry of a Half Adder is:
A) $A + B$ B) $A \oplus B$ C) $A'B$ D) AB
4. A Half Adder does not handle:
A) Carry-in B) Carry-out C) Sum D) XOR
5. Logic gates required to build a Half Adder:
A) XOR + AND B) OR + NOR C) XOR + NAND D) Only XOR
6. If $A=1, B=1 \rightarrow$ Sum=?
A) 0 B) 1 C) Undefined D) X
7. If $A=0, B=1 \rightarrow$ Carry=?
A) 0 B) 1 C) X D) Cannot determine
8. Half Adder is used in:
A) ALU B) Full Adder C) Multipliers D) All of these
9. A Full Adder adds:
A) 2 inputs B) 3 inputs (A, B, Cin) C) 4 inputs D) 1 input
10. Full Adder sum expression:
A) $A \oplus B \oplus Cin$ B) $AB + Cin$ C) $A + B$ D) $A \oplus B$
11. Carry-out of Full Adder:
A) $AB + BCin + ACin$ B) $A \oplus B$ C) $A'B$ D) $Cin'A$
12. Full Adder can be built using:
A) 2 Half Adders + OR B) 3 XOR gates only C) 1 NAND D) 1 NOR
13. For $A=1, B=1, Cin=1 \rightarrow$ Sum=?
A) 1 B) 0 C) X D) 3
14. Same inputs \rightarrow Carry-out=?
A) 0 B) 1 C) Undefined D) X

15. A chain of Full Adders creates a:
A) Decoder B) Ripple Adder C) Encoder D) Comparator
16. A 4-bit ripple adder uses:
A) 4 Full Adders B) 8 Full Adders C) 2 Half Adders D) 1 MUX
17. A multiplexer selects:
A) Multiple outputs → one input B) One input → many outputs C) Many inputs → one output D) None
18. A 4-to-1 MUX has:
A) 2 select lines B) 4 select lines C) 1 select line D) 3 select lines
19. 8-to-1 MUX has:
A) 4 select lines B) 2 C) 3 D) 1
20. MUX is also called:
A) Selector B) Distributor C) Decoder D) Comparator
21. The output equation for a 4:1 MUX:
A) $S + D_0$ B) $S'D_0 + S D_1$ C) $A + B + C$ D) none
22. MUX is used for:
A) Data routing B) Arithmetic C) Memory D) Power control
23. 2-to-1 MUX selects:
A) 1 of 2 inputs B) 2 of 4 C) 1 of 4 D) 4 of 1
24. Select lines determine:
A) Which input appears at output
B) Voltage levels
C) Speed
D) Fan-out
25. MUX is similar to:
A) Switch B) ALU C) Counter D) Comparator
26. A MUX implements Boolean functions by:
A) Forcing outputs to 0
B) Selecting minterms
C) Selecting memory
27. A 16-to-1 MUX needs:
A) 2 selects B) 4 selects C) 3 D) 5

28. MUX helps reduce:
A) Wiring complexity B) Memory C) Power D) Noise only
29. A DEMUX performs:
A) Many inputs → one output
B) One input → many outputs
C) Many → many
D) None
30. 1-to-4 DEMUX uses:
A) 4 select lines B) 2 select lines C) 3 D) 1
31. DEMUX is used for:
A) Data distribution B) Encoding only C) Memory addressing D) Both A & C
32. A DEMUX is also called:
A) Distributor B) Selector C) Inverter D) Adder
33. 1-to-8 DEMUX has:
A) 1 input, 3 selects, 8 outputs
B) 8 inputs, 1 output
C) 3 inputs, 8 selects
D) None
34. DEMUX sends the input to:
A) All outputs B) A selected output only C) No outputs D) 2 outputs
35. DEMUX is used in:
A) Communication systems
B) Encoders
C) Comparators
D) Adders only
36. Select lines choose:
A) Which output receives data B) Speed C) Voltage D) None
37. A DEMUX is the opposite of:
A) MUX B) Counter C) Flip-flop D) Encoder
38. DEMUX helps implement:
A) Decoders
B) Adder
C) Comparator
D) ALU