

Identify Each Logic gates by name,
and Complete Truth Table

OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

AND

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

qmp

$F \equiv A \oplus B$

NOR

A	B	$\bar{A}$	$\bar{B}$	F
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

NOR

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

NAND



A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

imp

$F \equiv A \text{ NAND } B$

NAND

A	B	$\bar{A}$	$\bar{B}$	F
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

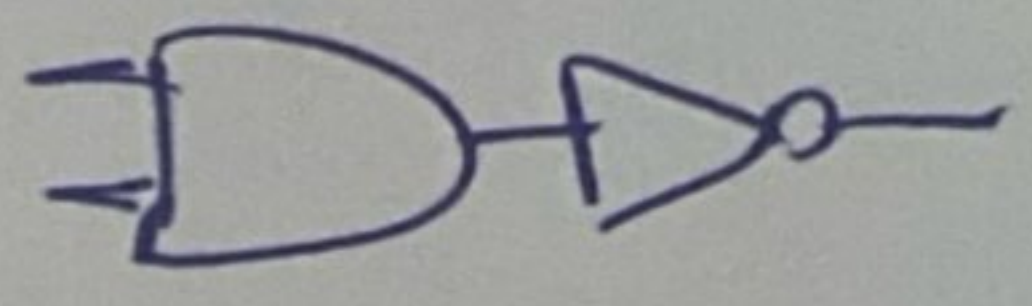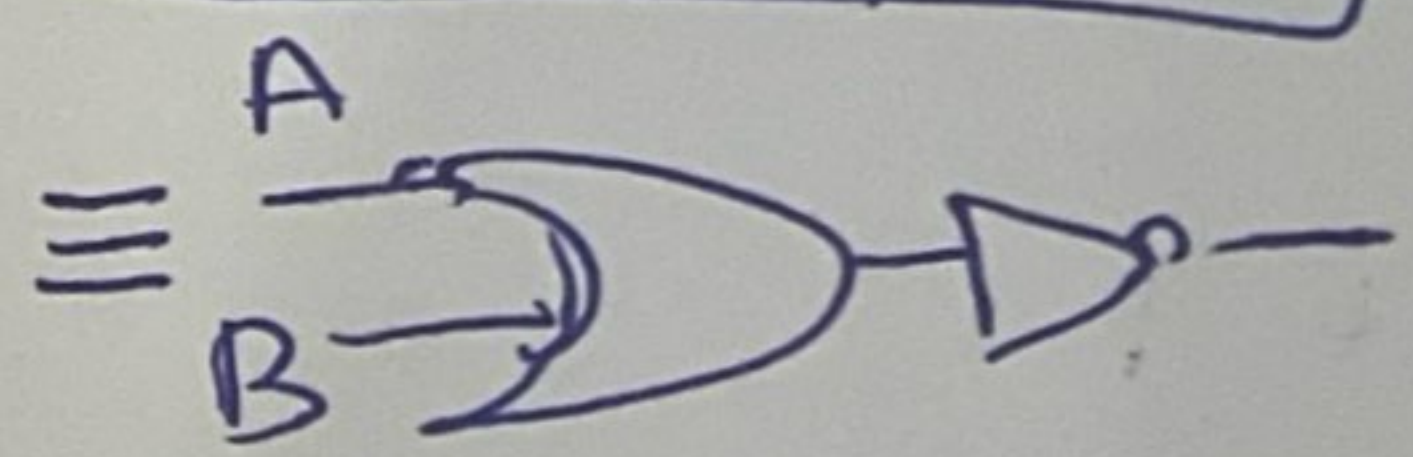

XOR

odd No of ones

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

NOT

A	F
0	1
1	0

$\bar{\bar{A}} = A$
 $\overline{A \text{ NAND } B} = A \text{ XOR } B$

Truth table

Rules

(2)

No of Rows = No of inputs

$$N(\underbrace{A, B, C}_{\text{3 inputs}}) \Rightarrow 2^{\textcircled{3}} = 8$$

$$N(\underbrace{A, B}_{\text{2 inputs}}) \Rightarrow 2^{\textcircled{2}} = 4$$

$$N(A, B, C, D) \Rightarrow 2^{\textcircled{4}} = 16$$

3 inputs
A, B, C

$$2^{\textcircled{3}} - 1 = 7$$

from 0 to $2^n - 1$

Example. $N(A, B, C)$ Range from 0 : 7

Example

We have a circuit that output 1 if ~~two~~^{two} or more input of A, B, C is 1

otherwise = 0. Find Truth Table

1) 3 inputs $\Rightarrow 2^3 = 8$ Rows

$$\boxed{0} \rightarrow \boxed{7}$$

2) Draw inputs

3) put outputs

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Sum-Of-Products & Product-Of-Sum

Output for last Example

is

$\bar{A}BC$

$A\bar{B}C$

$AB\bar{C}$

ABC

$F =$

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Sum of Products

$$F = \sum m(3, 5, 6, 7)$$

or

$$F = \prod M(0, 1, 2, 4)$$



$$(\bar{A}+B+C)(A+\bar{B}+\bar{C})(A+\bar{B}+C)(\bar{A}+B+\bar{C})$$

Product of Sum

$\bar{A}$	B	C	F	
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	0	m_2
0	1	1	1	m_3
1	0	0	0	m_4
1	0	1	1	m_5
1	1	0	1	m_6
1	1	1	1	m_7

De Morgan's Theorem.

4

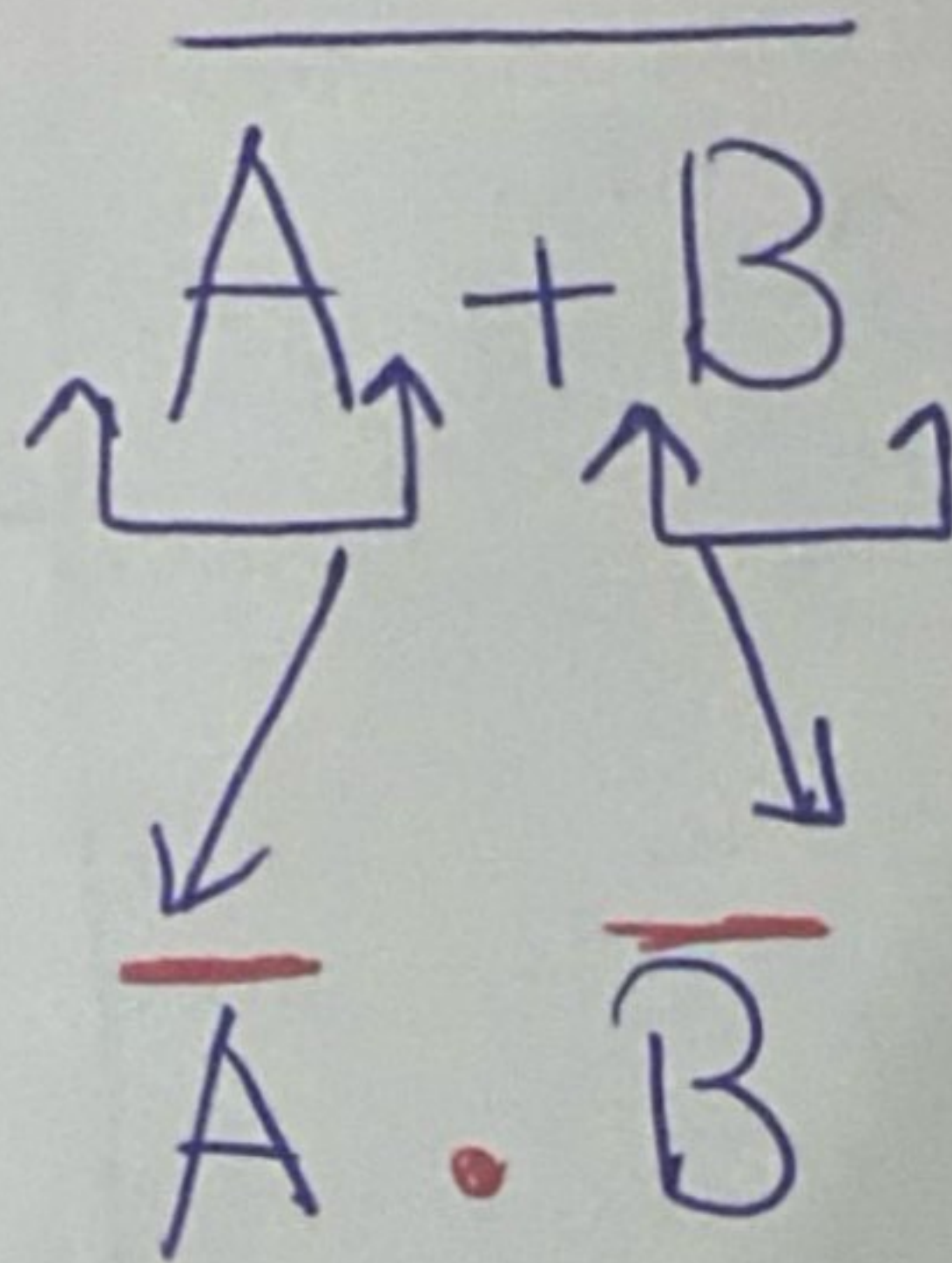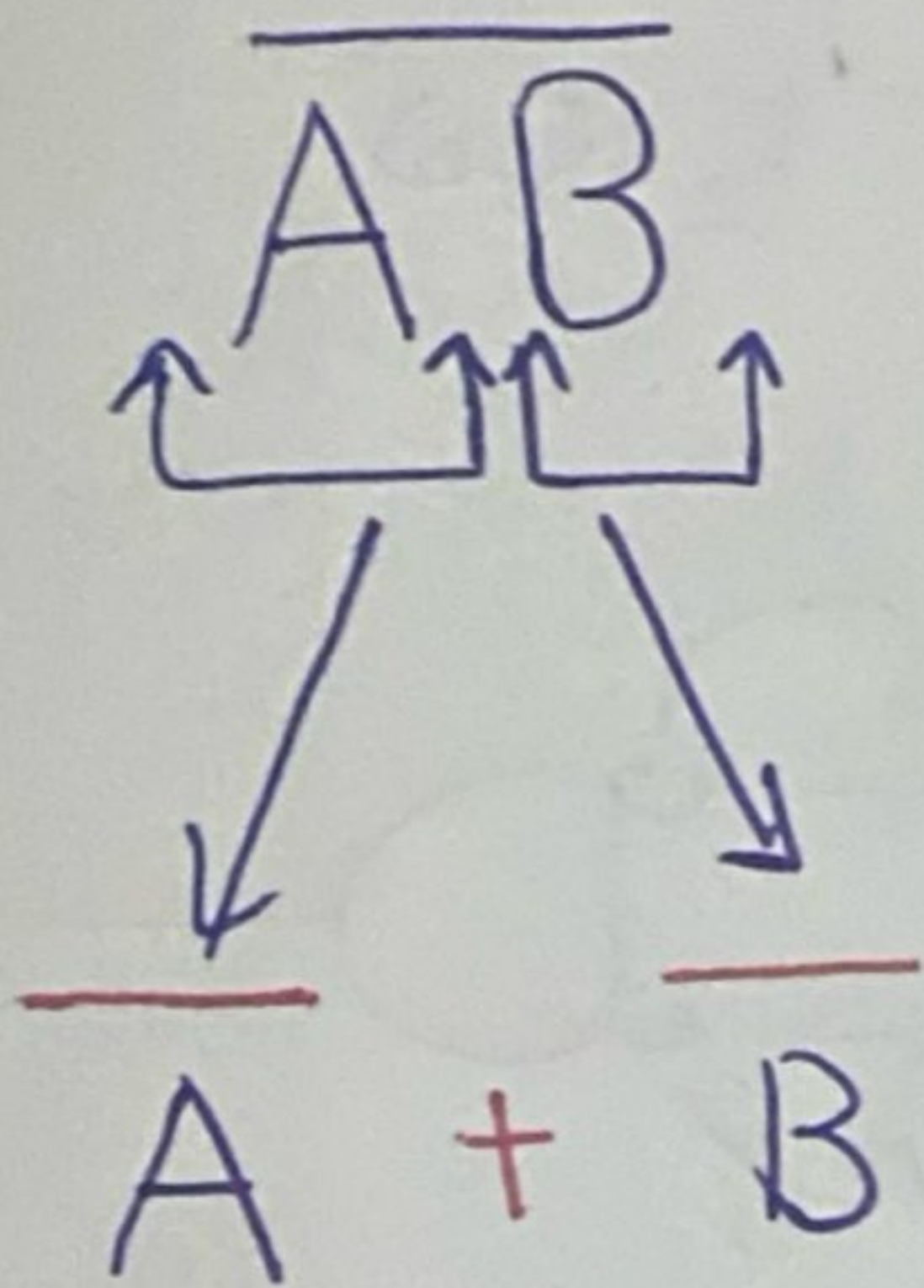

Note ① → Move ——— To inputs

② → + → • • → +

→ Apply again if needed!

Example

$$\overline{A + \overline{BC}}$$

$$\Rightarrow \overline{A} \cdot \overline{\overline{BC}}$$




$$\Rightarrow \overline{A} \cdot BC \Rightarrow \overline{A}BC$$

#

$$\overline{\overline{A}} = A$$


#

graphical demorgan

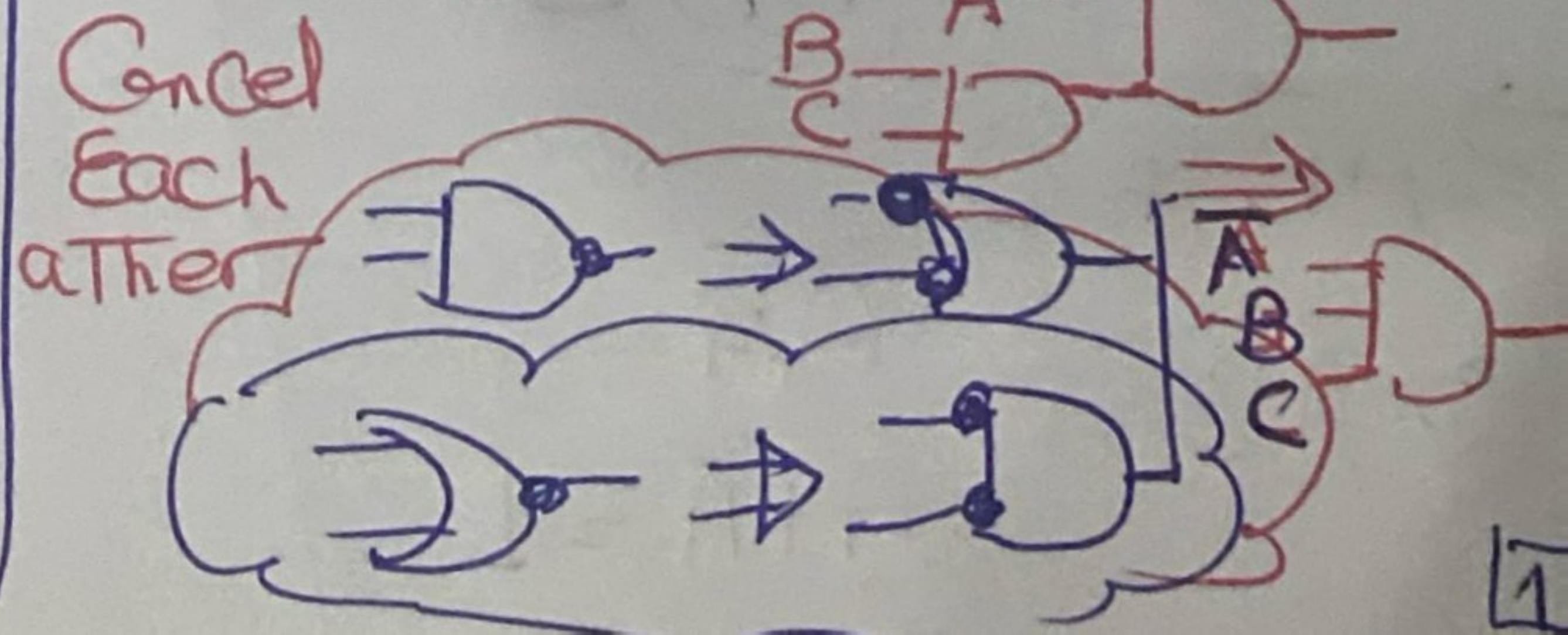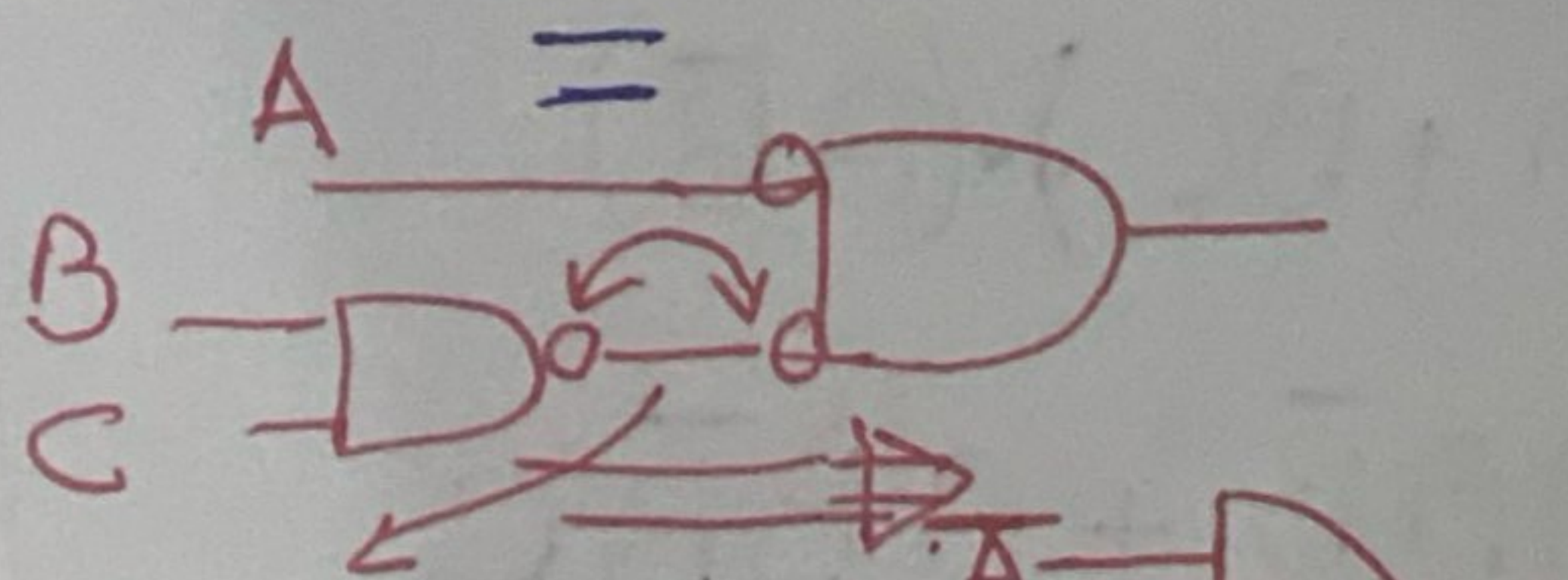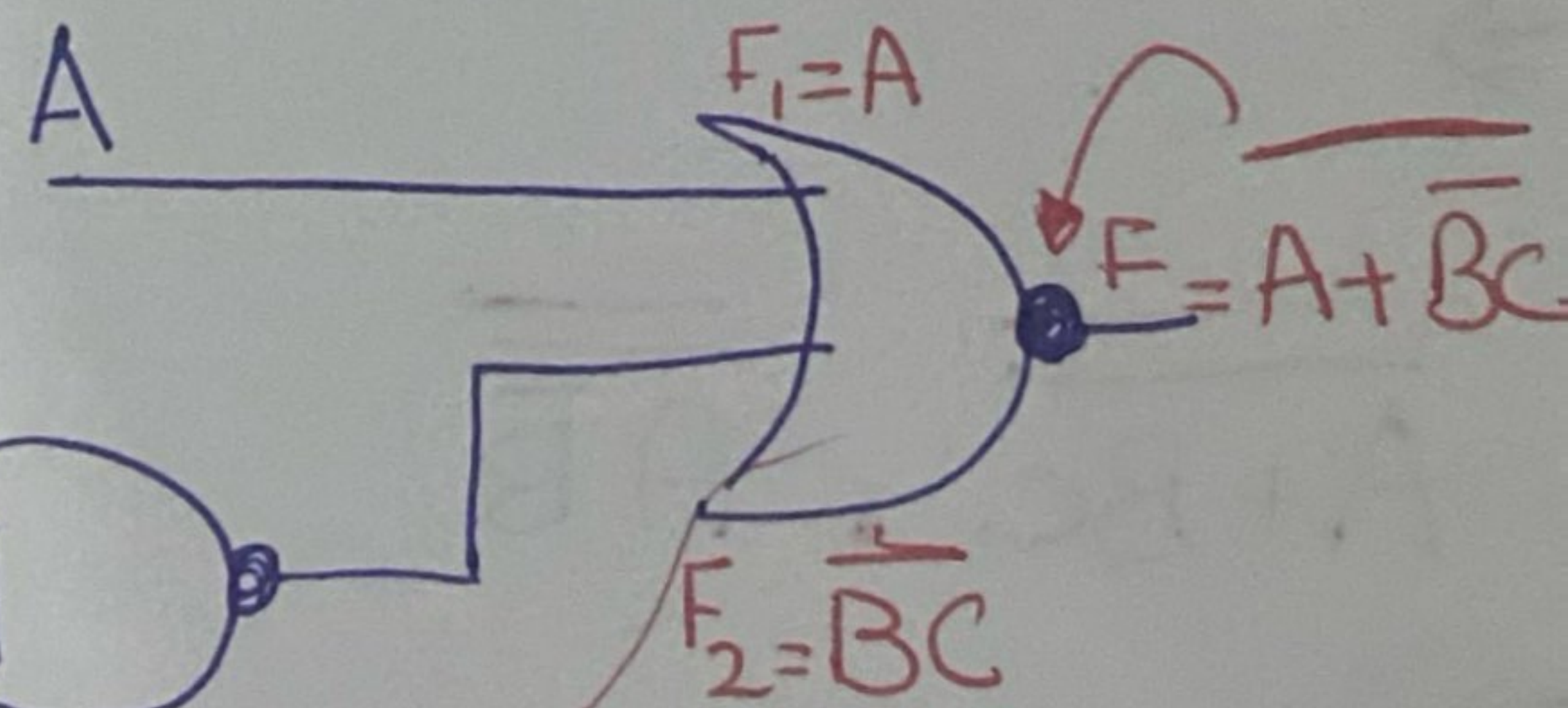

Example


(5)

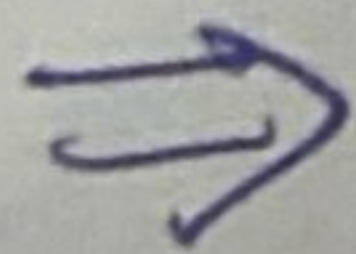

$$\overline{AB + CD}$$


$$(\overline{AB}) \cdot (\overline{CD})$$
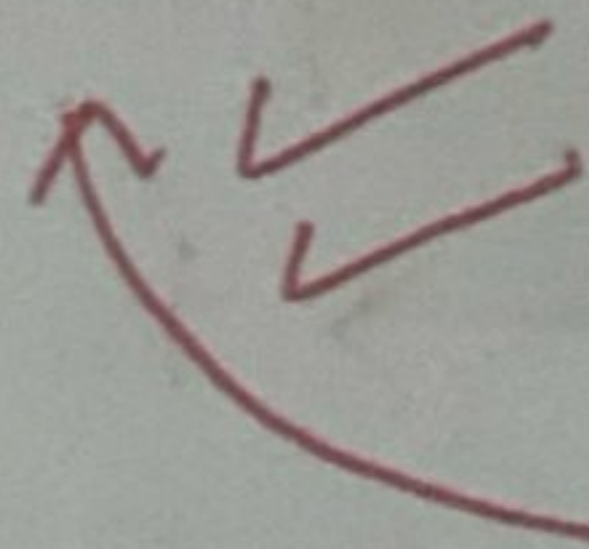
$$(\overline{A + B}) \cdot (\overline{C + D})$$




Example

$$\overline{A + BC + A\overline{B}}$$

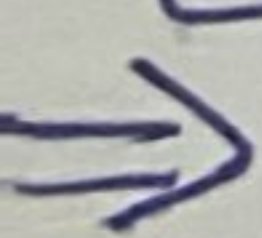
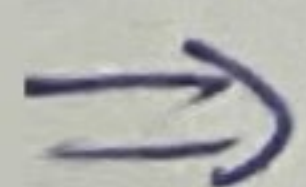
$$\overline{A + BC} \cdot \overline{A\overline{B}}$$



$$(A + BC) \cdot (A\overline{B})$$


$$A\overline{B} + A\overline{B}BC$$

$$A\overline{B} + 0$$


$$A\overline{B}$$

$$\begin{aligned} A\overline{A} &= 0 \\ A + \overline{A} &= 1 \end{aligned}$$






graphical demorgan

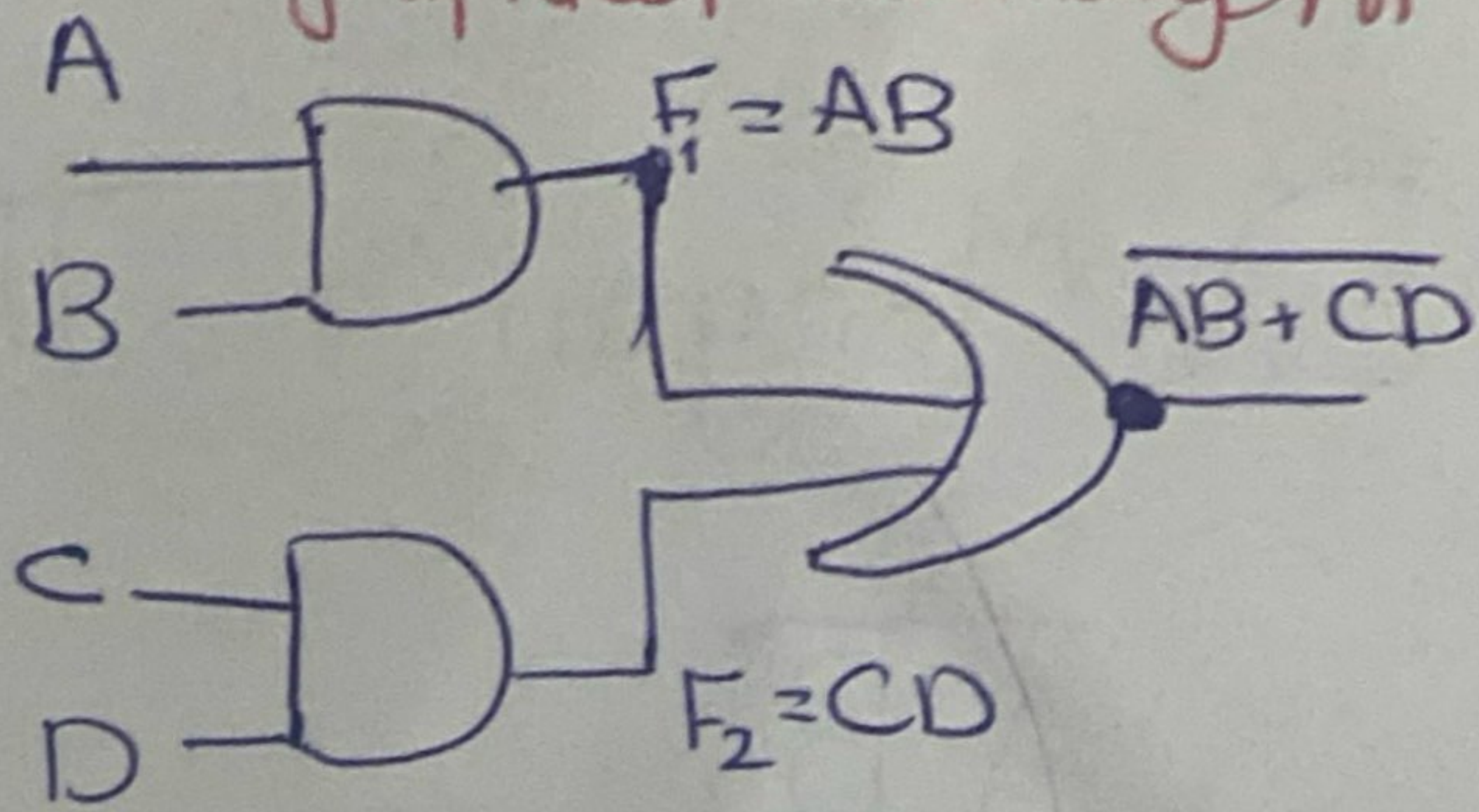

=

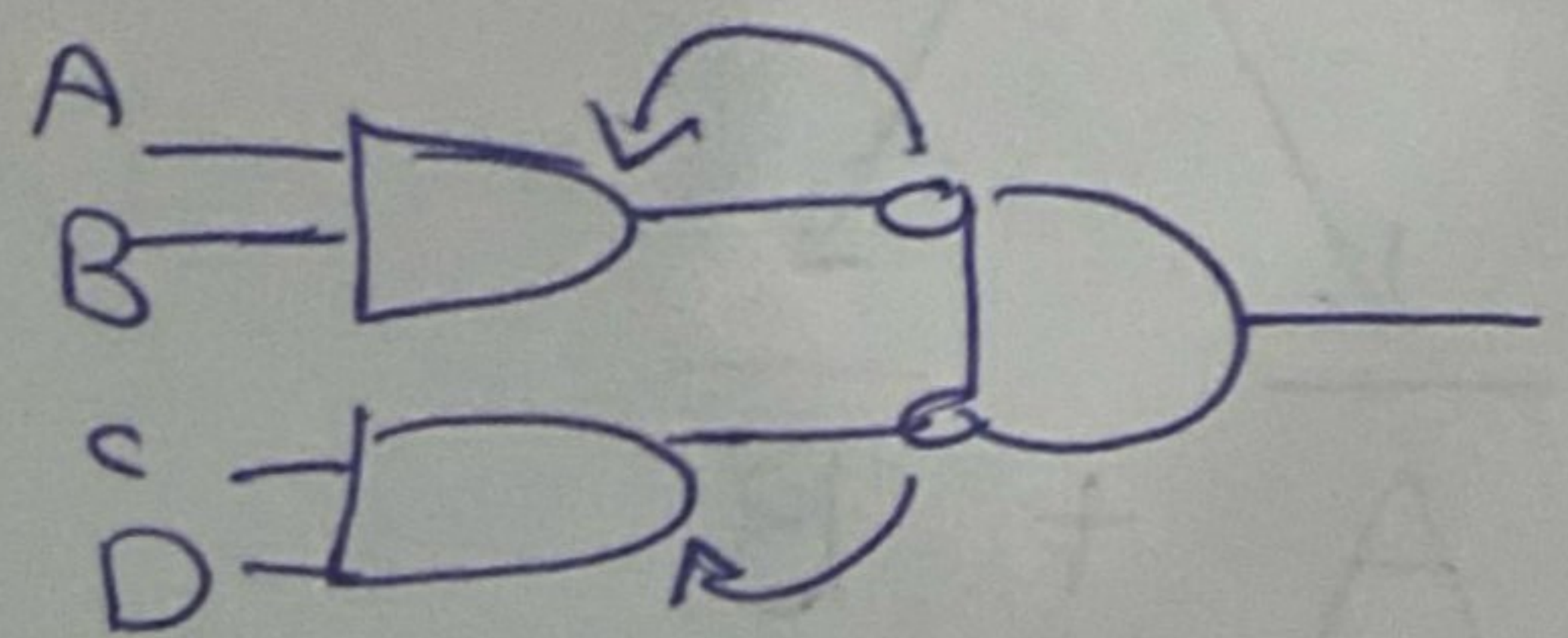

=

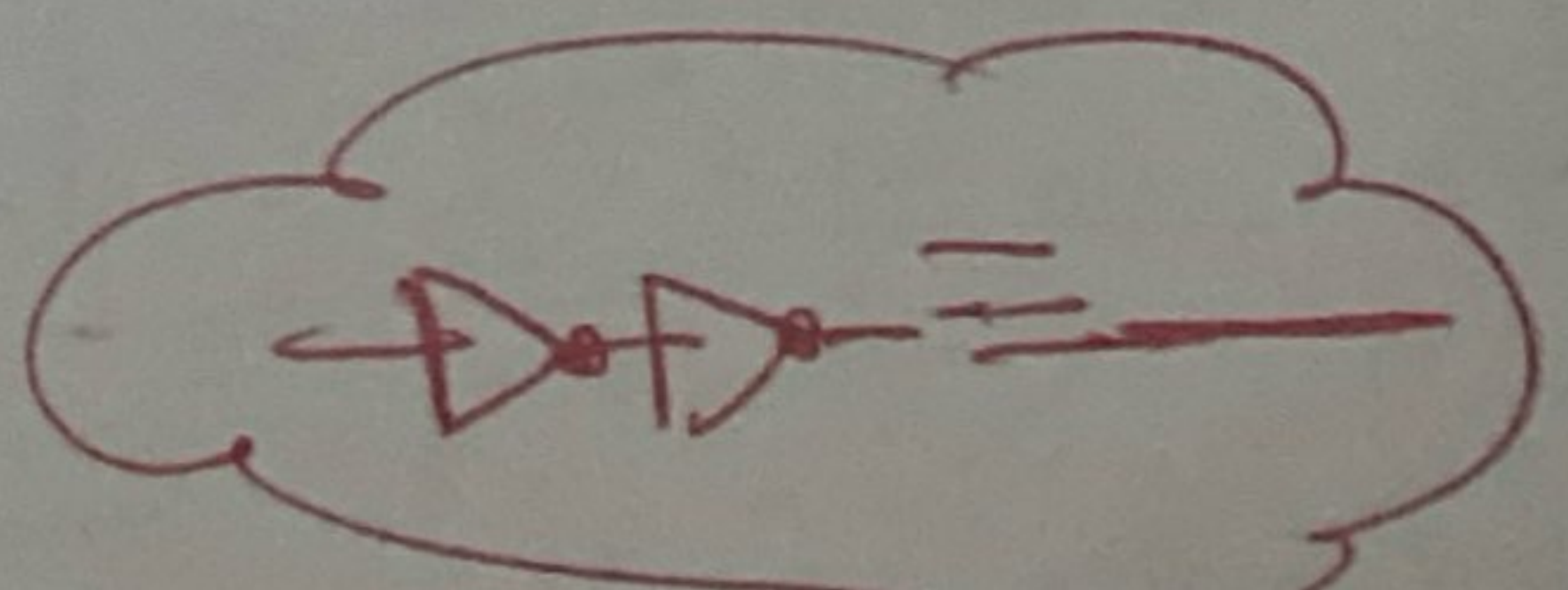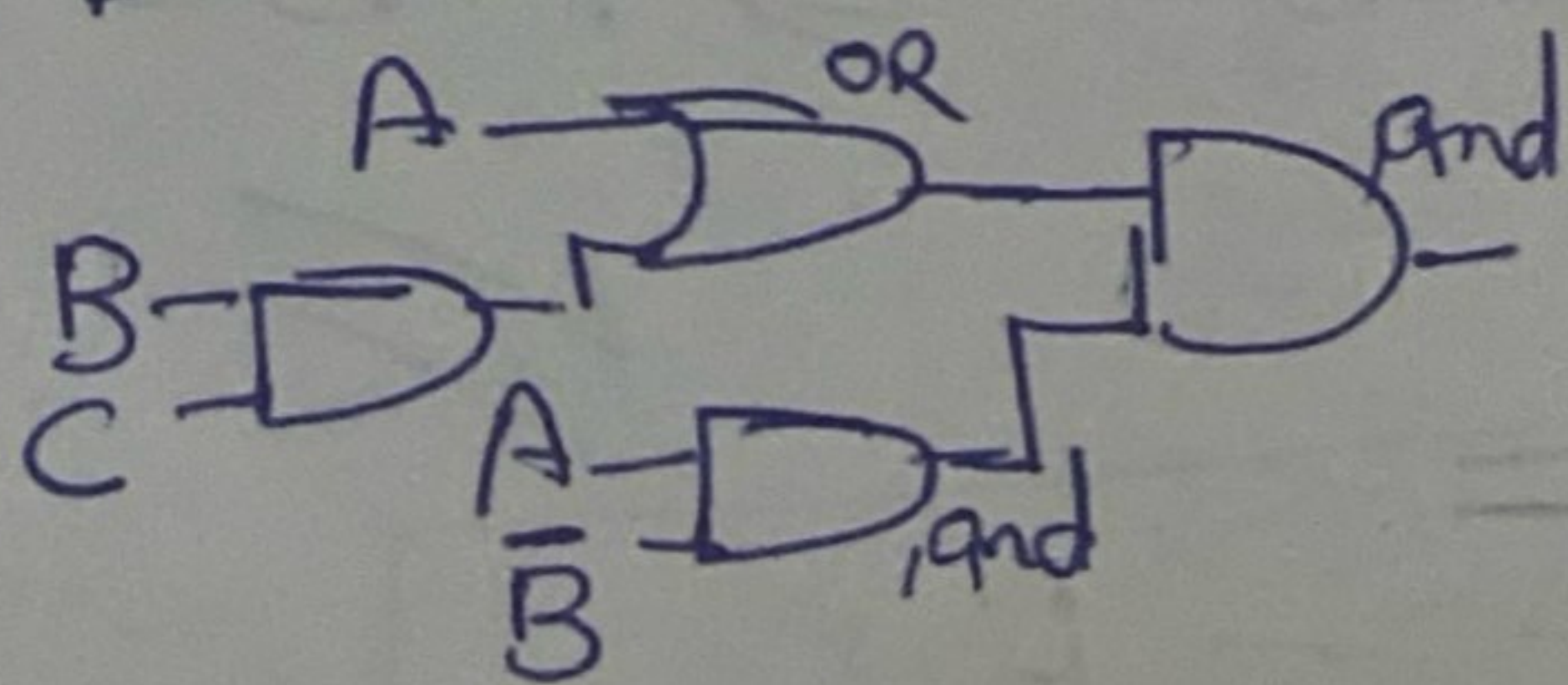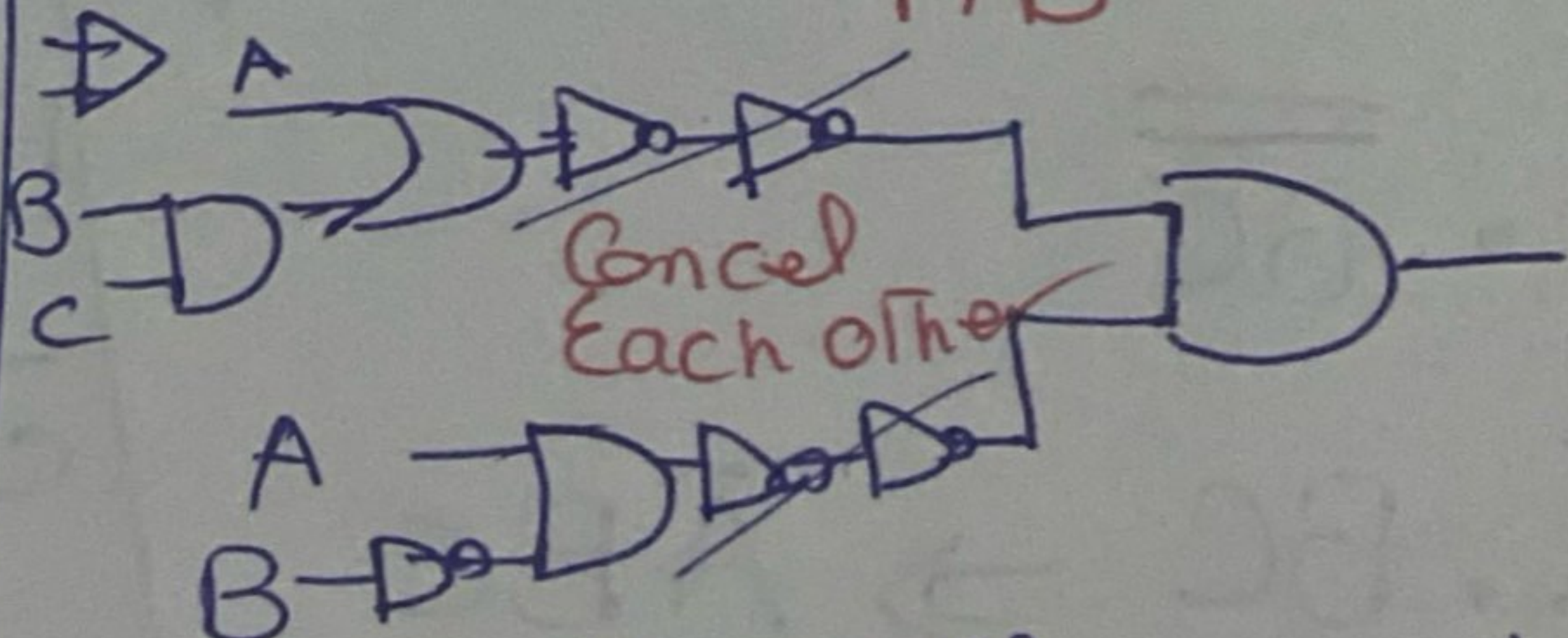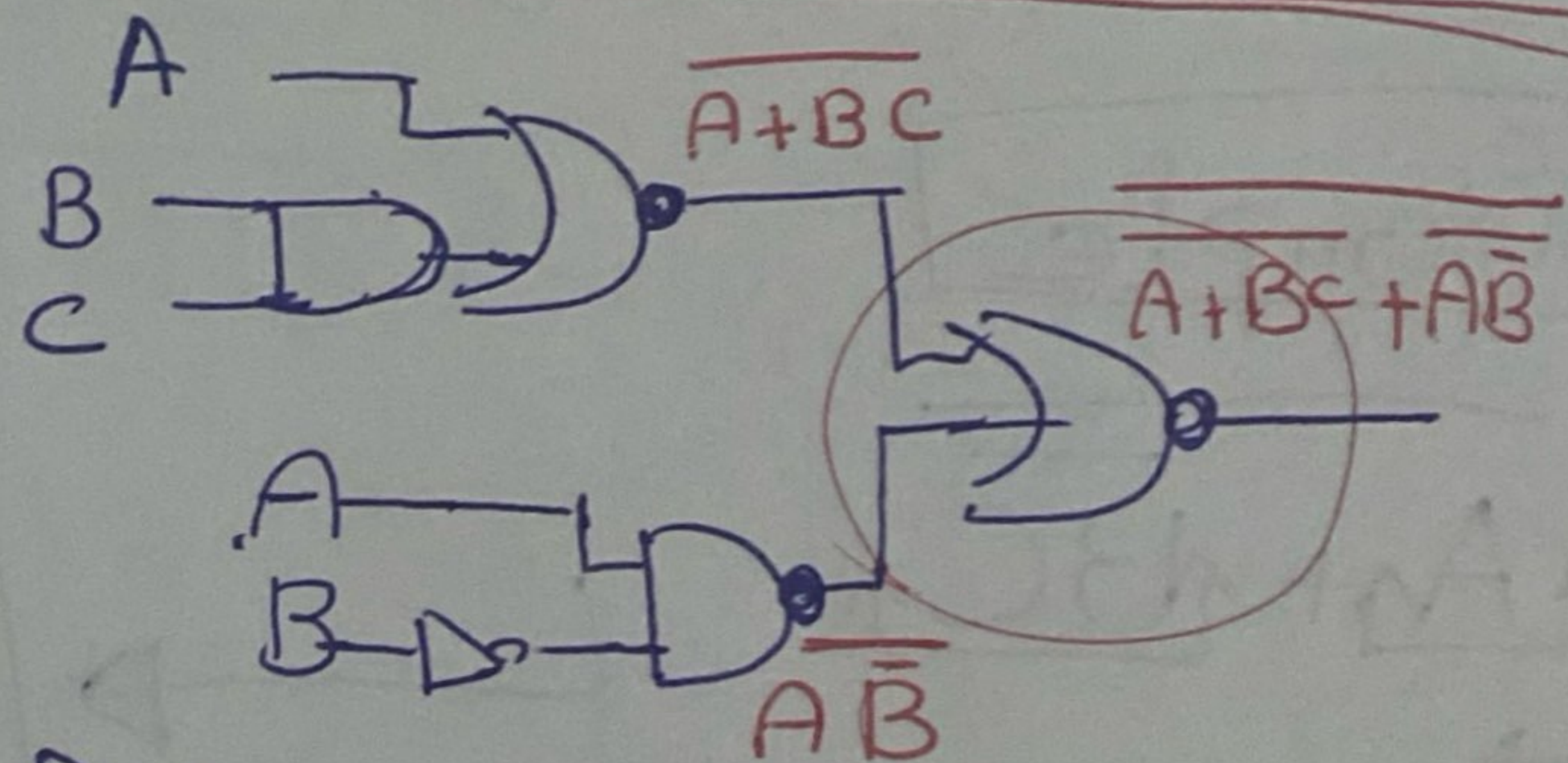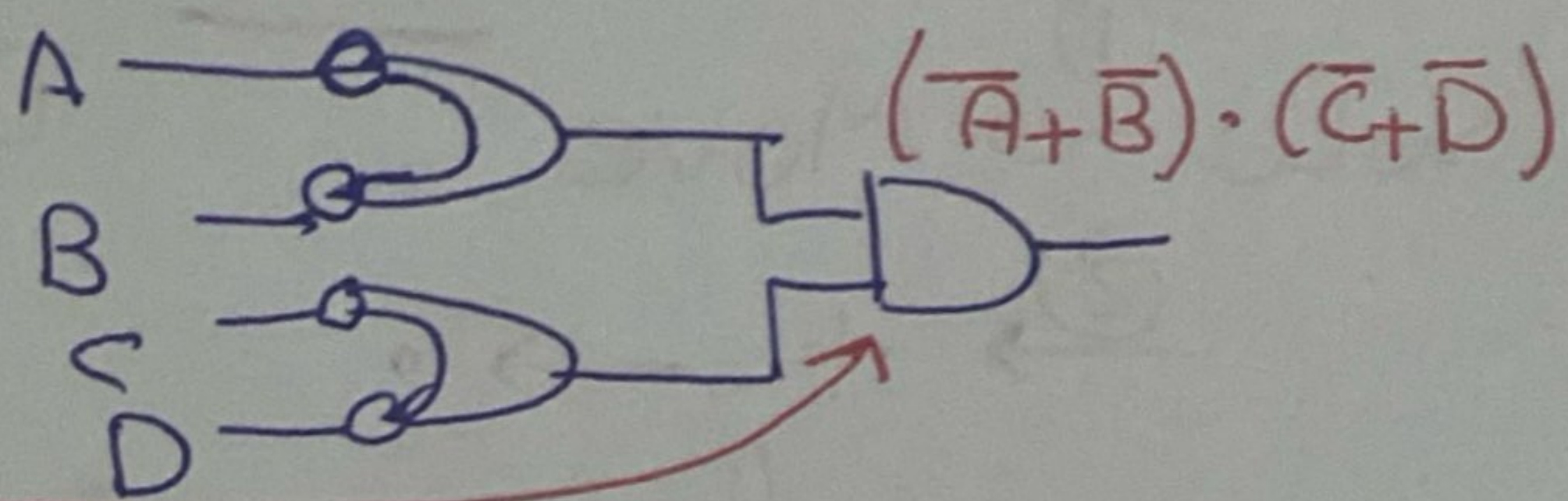

What is Complement

$$\text{Complement} = F' = \overline{F}$$

Find the Complement of $F = A + BC + \overline{A}\overline{B}$

Sol

$$F' = \overline{F} = \overline{A + BC + \overline{A}\overline{B}}$$

Complement

$$= \overline{A} \cdot \overline{BC} \cdot \overline{\overline{A}\overline{B}}$$

$$= \overline{A} \cdot (\overline{B} + \overline{C}) \cdot (\overline{\overline{A}} + \overline{\overline{B}})$$

$$= \overline{A} \cdot (\overline{B} + \overline{C}) \cdot (A + B)$$

$$= (\overline{A}\overline{B} + \overline{A}\overline{C}) \cdot (A + B)$$

$$= (\overline{A}\overline{B}) + (\overline{A}\overline{C})$$

$$= \overline{A}\overline{B}\overline{B} + \overline{A}\overline{B}\overline{C}$$

$$= (\overline{A} \cdot 0) + \overline{A}\overline{B}\overline{C}$$

$$\boxed{= \overline{A}\overline{B}\overline{C}} \quad \#$$

We can use
demorgan
here

To
Simplify

What is Dual?

7

Change $0 \rightarrow +$ $1 \rightarrow \cdot$ $0 \rightarrow 1$ $1 \rightarrow 0$ $A \rightarrow \bar{A}$
 $\bar{A} \rightarrow A$

Find

1) Complement of Function $F = A + BC + \bar{A}\bar{B}$

$$\bar{F} = \overline{A + BC + \bar{A}\bar{B}} = \bar{A} \bar{B} \bar{C}$$

↳ solved before $\neq$

2) Find dual

$$F^D = A \cdot (B + C) \cdot (\bar{A} + \bar{B})$$

Same.

3) Find Complement from dual.

Change only $\bar{A} \rightarrow A$ $\bar{B} \rightarrow B$ $\bar{C} \rightarrow C$

From dual

$$F = A'(\bar{B} + \bar{C})(\bar{\bar{A}} + \bar{\bar{B}})$$

$$= (A'B' + A'C')(A + B)$$

$$= \underset{0}{AA'B'} + \underset{0}{A'B'B} + \underset{0}{AA'C'} + A'C'B$$

$$= 0 + \underset{0}{A'B'B} + 0 + A'BC' = \boxed{A'BC'} \neq$$

Karnaugh Mapping K-maps

use this truth table to find simplified

function of 3 inputs

Rule

- [1] large group
- [2] group of 1, 2, 4, 8, ...
- [3] Don't leave any 1 alone

	A	B	C	F
0	0	0	0	1
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

note

	BC	00	01	11	10
A	0	1	1	1	0
1		0	1	0	0

$F = \bar{A}\bar{B} + \bar{B}C + \bar{A}C$

Examples

A \ BC	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$$F = \bar{C}$$

A \ BC	00	01	11	10
0	1	1	1	1
1	1	0	0	1

$$F = \bar{C} + \bar{A}$$

A \ BC	00	01	11	10
0	0	1	1	0
1	1	0	0	1

$$F = A\bar{C} + \bar{A}C$$

A \ BC	00	01	11	10
0	1	0	0	1
1	1	0	0	0

$$F = \bar{B}\bar{C} + \bar{A}\bar{C}$$

A \ BC	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$F = \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC + \bar{A}B\bar{C}$$

A \ BC	00	01	11	10
0	1	1	0	0
1	0	0	1	1

$$F = \bar{A}\bar{B} + AB$$