



جامعة برج العرب التكنولوجية  
BORG AL ARAB TECHNOLOGICAL UNIVERSITY

# Digital Engineering

Assoc. Prof. Osama Elnahas, Dr. Dina Abdelhafiz  
Dr. Bassant Tolba, Dr. Radwa Rady

Second Year –Information Technology Program  
Fall 2025

# Lecture 10

## What is an S-R Latch?


### A latch

- ▶ Is an **asynchronous circuit** (it doesn't require a clock signal to work).
- ▶ Has two stable states, HIGH ("1") and LOW ("0")
- ▶ Can be used for storing binary data.
- ▶ Sequential circuits and larger storage devices, such as **shift registers**, use latches as their principal building block.

## Set-Reset (S-R) latch


- ▶ The simplest latch is the **Set-Reset (S-R) latch**. You can build one by connecting two **NOR gates** with a cross-feedback loop.
- ▶ This feedback path is important to storing one bit of data as long as the circuit is powered.

Input S	Input R	Output Q
0	0	Previous State
0	1	0
1	0	1
1	1	o (Invalid)

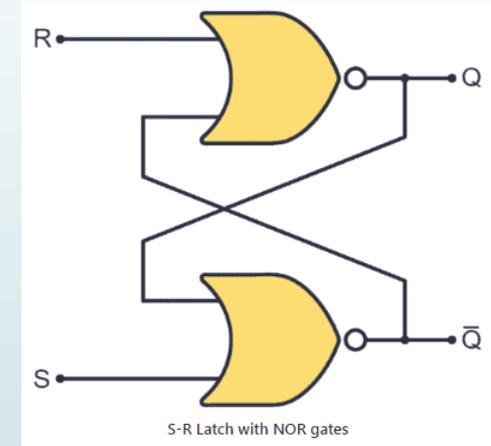


- ▶ Remember that the NOR gate only gives “1” when both inputs “0”,

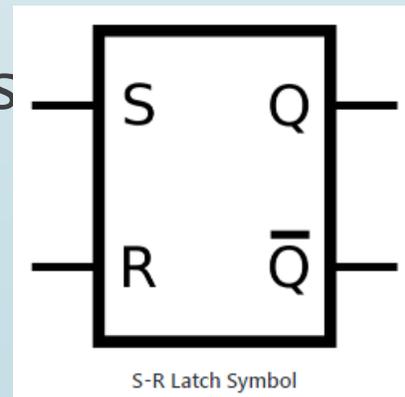with any other input combination the output is “0”



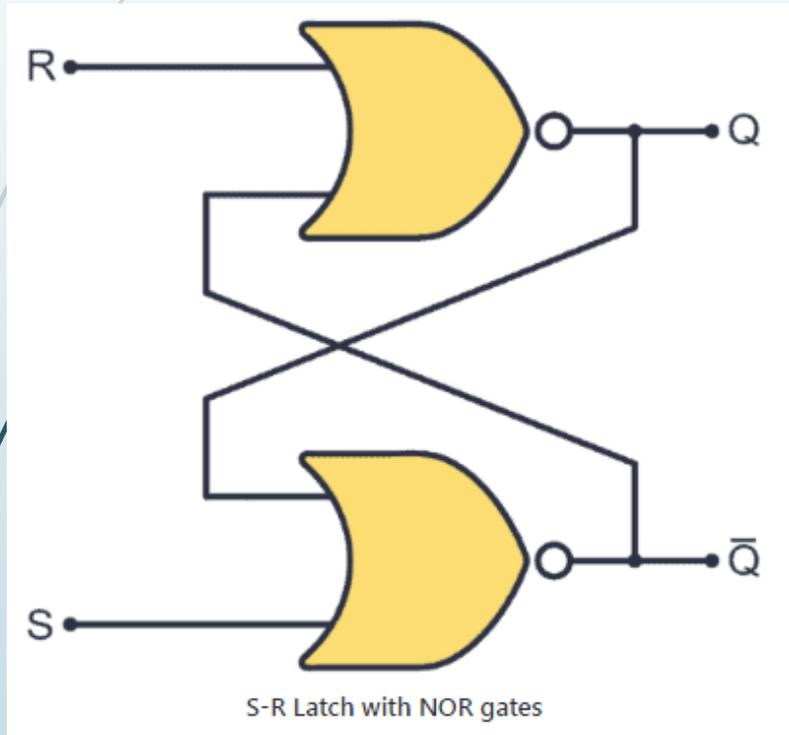
## SR LATCH

The S-R Latch can also be built two NOR gates with a cross-feedback loop.



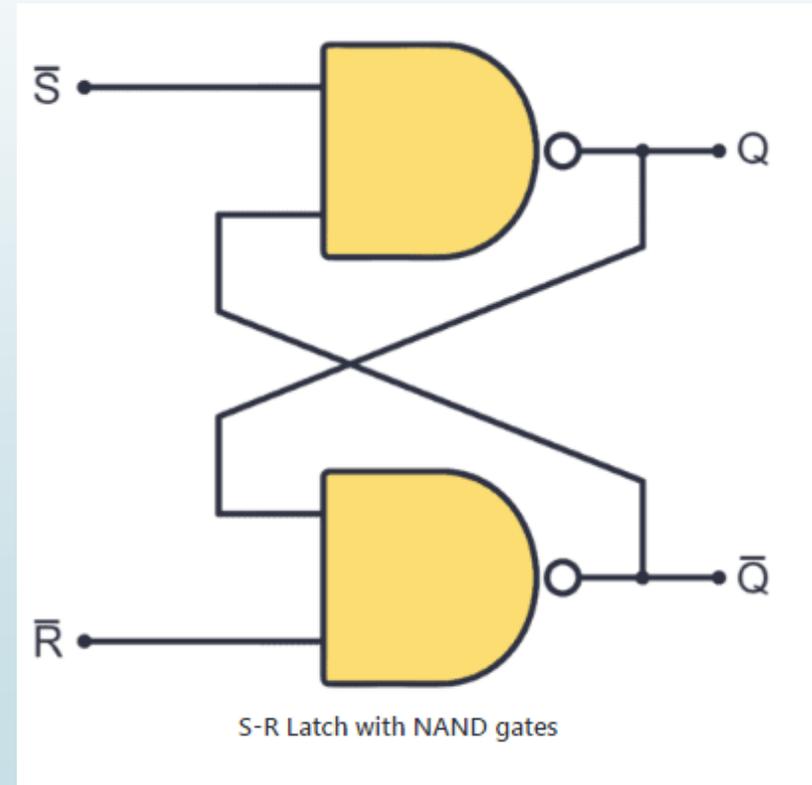
The S-R Latch can also be built using two NAND gates with a cross-feedback loop


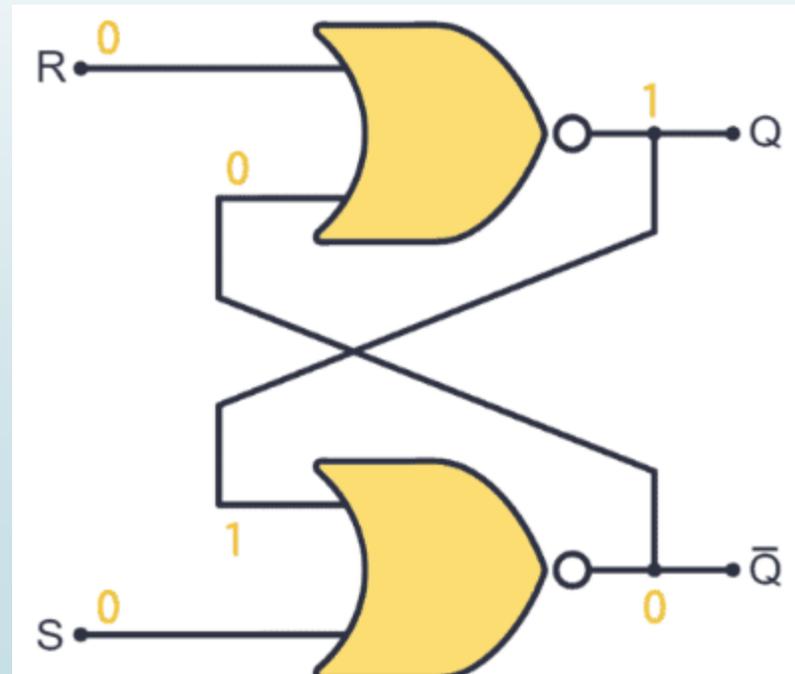
## How SR LATCH works?

Suppose the Q output is “1” in the present state.


- ▶ If you now place both inputs in “0”, then the output will remain “1” as follows:
- ▶ This is the memory function of the S-R latch because it saves the previous value.



# How to reset the SR LATCH?

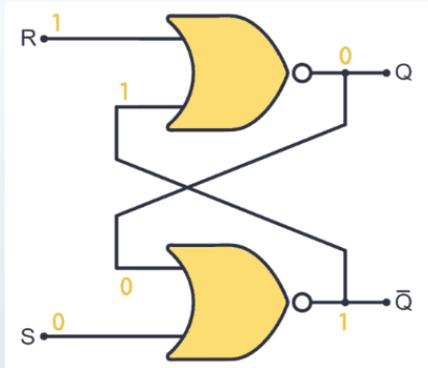
## HOW TO “Reset” the Q output to “0”?

as you can see in the truth table, you need a “1” in the R input and a “0” in the S input.



Input S	Input R	Output Q
0	0	Previous State
0	1	0
1	0	1
1	1	o (Invalid)

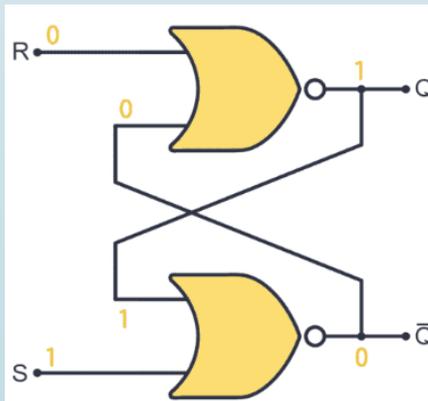But, if you want to “Set” a “1” in the Q output just follow the truth table and place a “1” in the S input and a “0” in the R input.



# WHEN $S=1$ , $R=1$ , $Q$ and $Q'$ both are 0!!!

## INVALID STATE

- ▶ Finally, the S and R inputs **should never be “1” at the same time** because the NOR gate only gives “1” when both of its inputs are “0”, but if one input is “1”, then the output will be “0”.
- ▶ As a result, **if S and R are “1”**, both latches’ outputs will be **“0” at the same time**, something **that violates this latch’s working principle.**


Input S	Input R	Output Q
0	0	Previous State
0	1	0
1	0	1
1	1	0 (Invalid)

## what is D latch

- The D Latch is a logic circuit most frequently used **for storing data in digital systems.**
- It is based on the S-R latch, **but it doesn't have an "undefined" or "invalid" state problem.**
- A **D latch** can store a bit value, either 1 or 0. When its Enable pin is HIGH, the value on the **D pin** will be stored on **the Q output.**
- It builds upon the design of the S-R latch, with a few added logic gates.
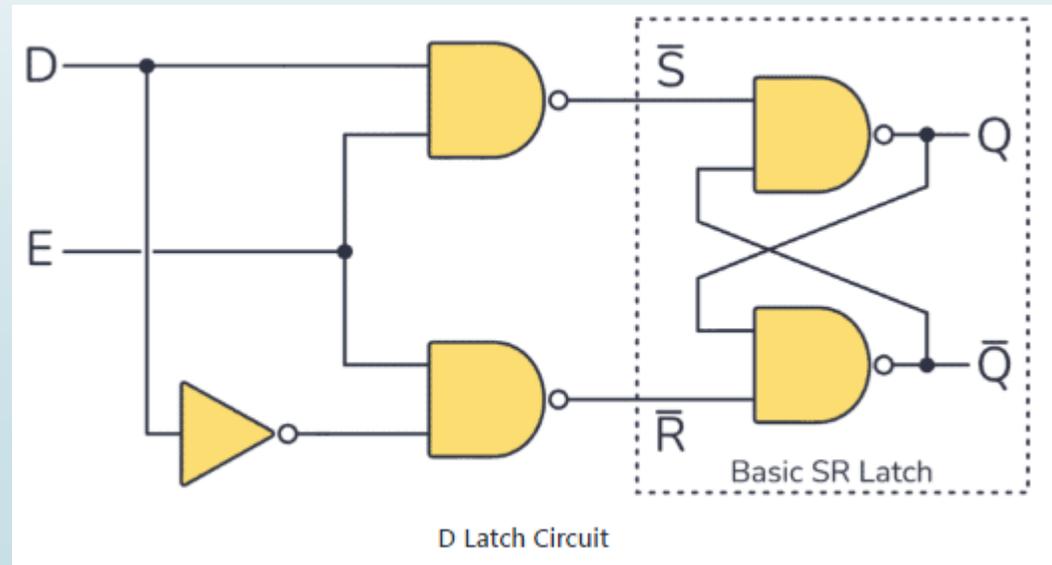
## D Latch circuit

You can see a D Latch circuit based on the S-R latch built with **NAND gates** below:



# Applications of Latches


- ▶ The latches find several applications in the field of digital electronics. They are most elementary storage components used to store one bit of information in digital systems.
- ▶ Latches are used as 1-bit memory element in digital systems.
- ▶ Latches are used to design digital registers which are employed for storage and manipulation of data in microprocessors and microcontrollers.
- ▶ Latches are used to design flip-flops which are basically the synchronized latches.
- ▶ Latches are also used in communication systems for temporary data storage or buffering purposes.

## What's the Difference Between Latch and Flip Flop?


- The terms *latch* and *flip flop* both can store a bit (1 or 0) at their outputs.
- While a *latch* can change its output at any time as long as it's enabled
- a *flip flop* is an edge-triggered device that needs a clock transition to change its output.
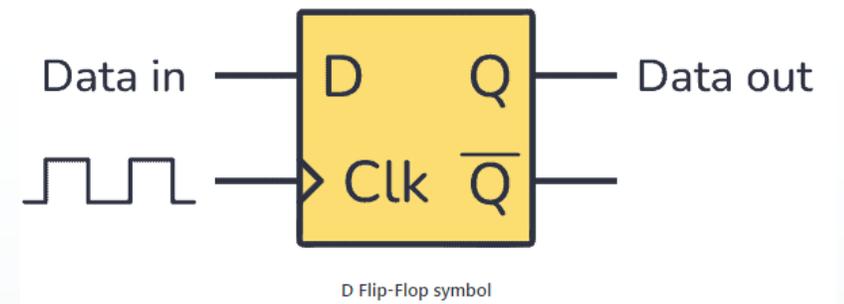
## The D Flip-Flop



- ▶ The D Flip-Flop is an edge-triggered circuit that combines a pair of D latches to store one bit.
- ▶ a basic building block in digital electronics to create counters or memory blocks such as shift registers.
- ▶ flip-flops are **synchronous circuits** that need **a clock signal (Clk)**.
- ▶ The D Flip-Flop will only store a new value from the D input when the clock goes from 0 to 1 (rising edge) or 1 to 0 (falling edge).




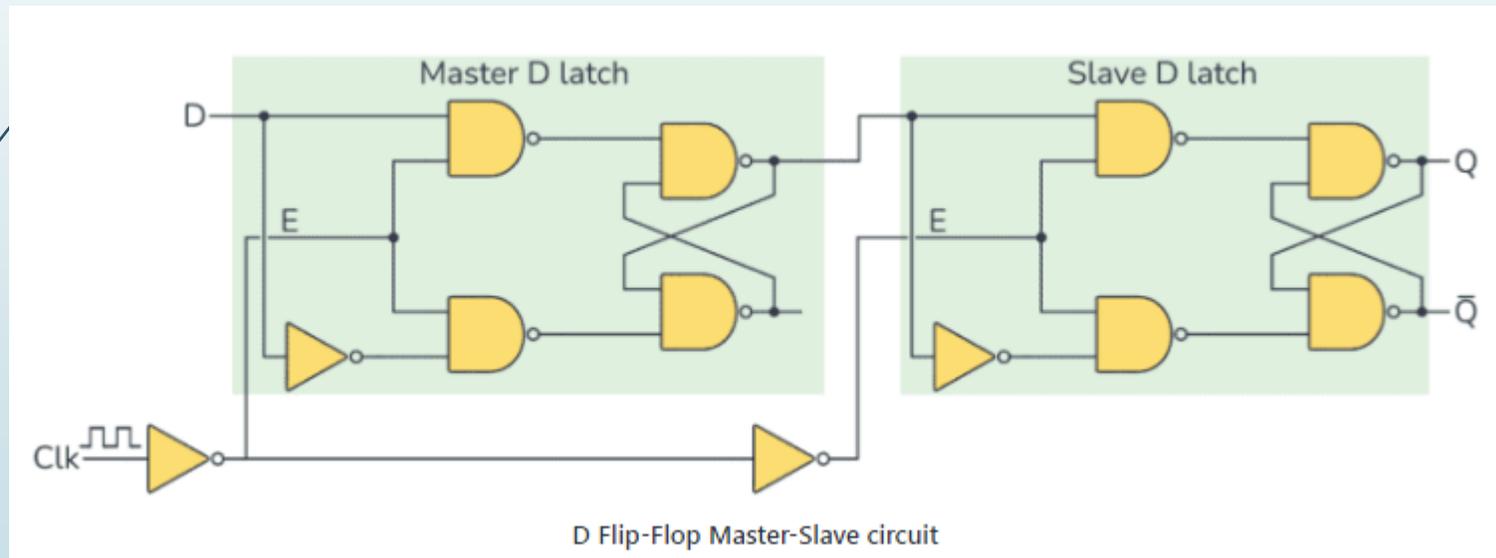A D Flip-Flop is built from **two D latches**.



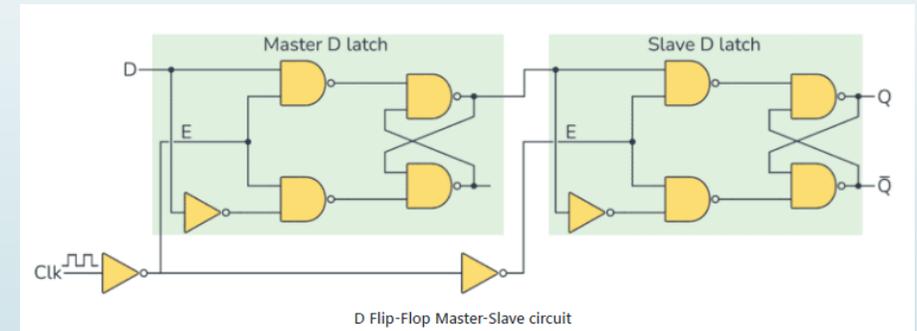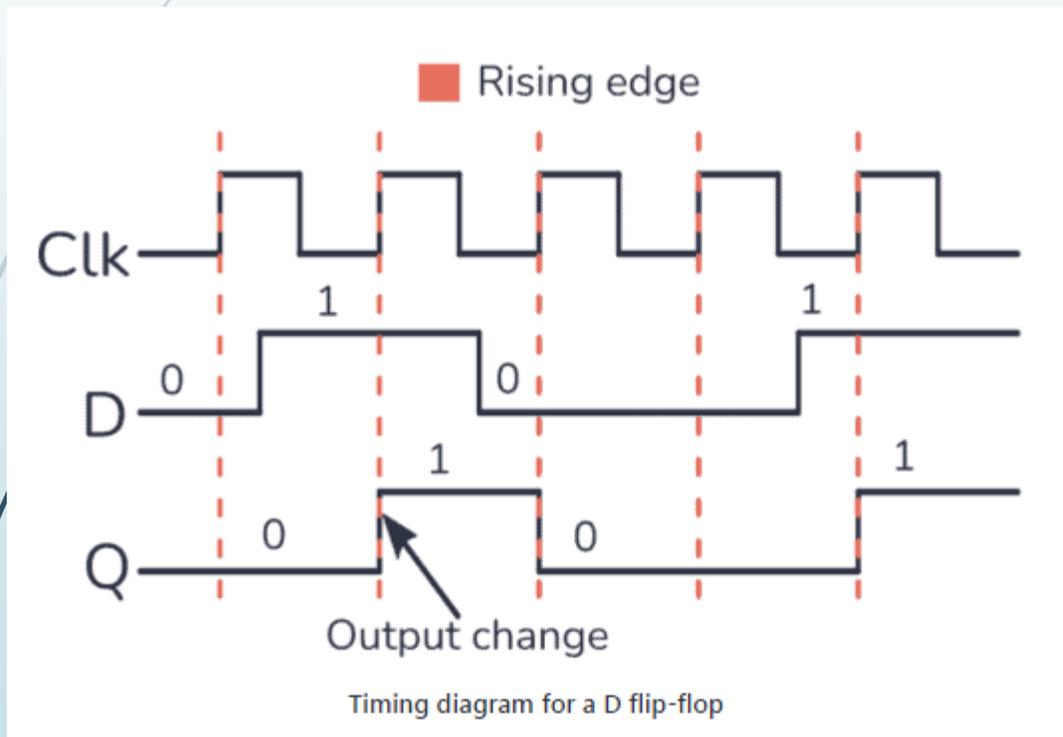- The output Q only changes to the value the D input has at the moment the clock goes from 0 to 1.



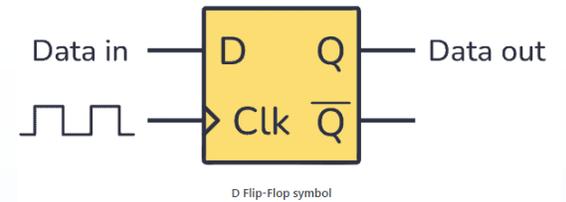


16

## What Can You Use Them For?


- The D Flip-flop is a very useful circuit. You can combine several D flip-flops to create for example **shift registers and counters**.
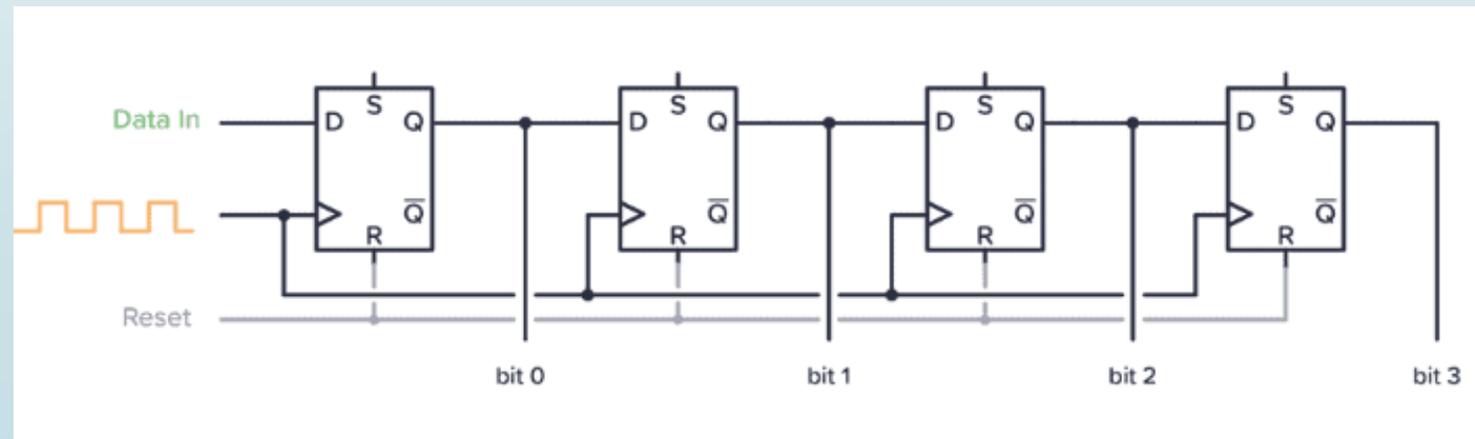
### Circuit Example: Shift Registers



- To create a shift register, connect the output of one flip-flop to the input of the next. New bits go into the first flip-flop on the left. And for every clock pulse, the bits stored in the other flip-flops are shifted one place to the right.



# Shift register

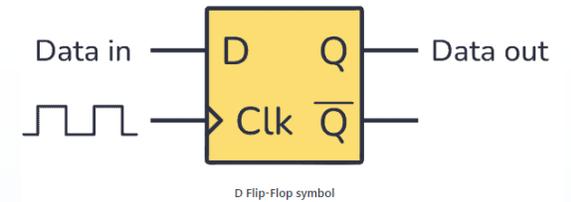

- ▶ A shift register is a common building block in digital electronics that is used to store and move bits,
- ▶ What is a shift register used for? A shift register is commonly used in data storage, data movement, and data manipulation.
- ▶ The number of bits you can store in a shift register is equal to the number of flip-flops used.
- ▶ To create a shift register, connect the output of one flip-flop to the input of the next. New bits go into the first flip-flop on the left. And for every clock pulse, the bits stored in the other flip-flops are shifted one place to the right.

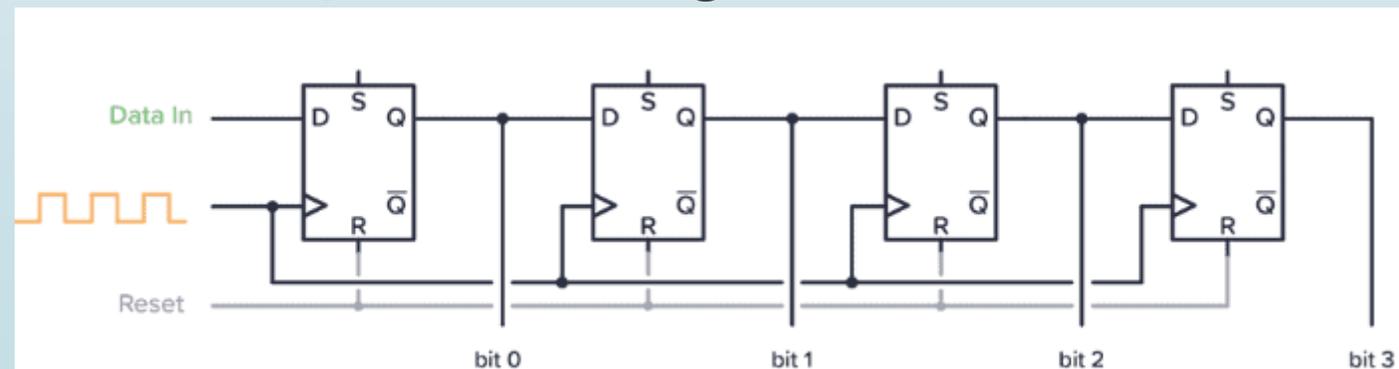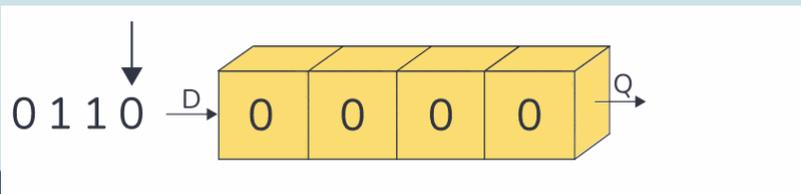

## Shift register Applications


- ▶ Shift register is used as **Parallel to serial converter**, which converts the parallel data into serial data. It is utilized at the transmitter section after Analog to Digital Converter (ADC) block.
- ▶ Shift register is used as **Serial to parallel converter**, which converts the serial data into parallel data. It is utilized at the receiver section before Digital to Analog Converter (DAC) block.
- ▶ Shift register along with some additional gate(s) generate the sequence of zeros and ones. Hence, it is used as **sequence generator**.
- ▶ Shift registers are also used as **counters**.

## The JK Flip-Flop

- ▶ Flip-flops are components that can store a digital value on their output. They have a Clock input (Clk) which determines when they can change the state of their output.
- ▶ The JK Flip-Flop is a type of flip-flop that can be set, reset, and toggled. It can be used for **making counters, event detectors, frequency dividers.**
- ▶ **Toggle** means that switching in the output instantly i.e.  $Q=0, Q'=1$  will immediately change to  $Q=1$  and  $Q'=0$  and this continuation keeps on changing. 0-1-0-1-0-1-0-1.....
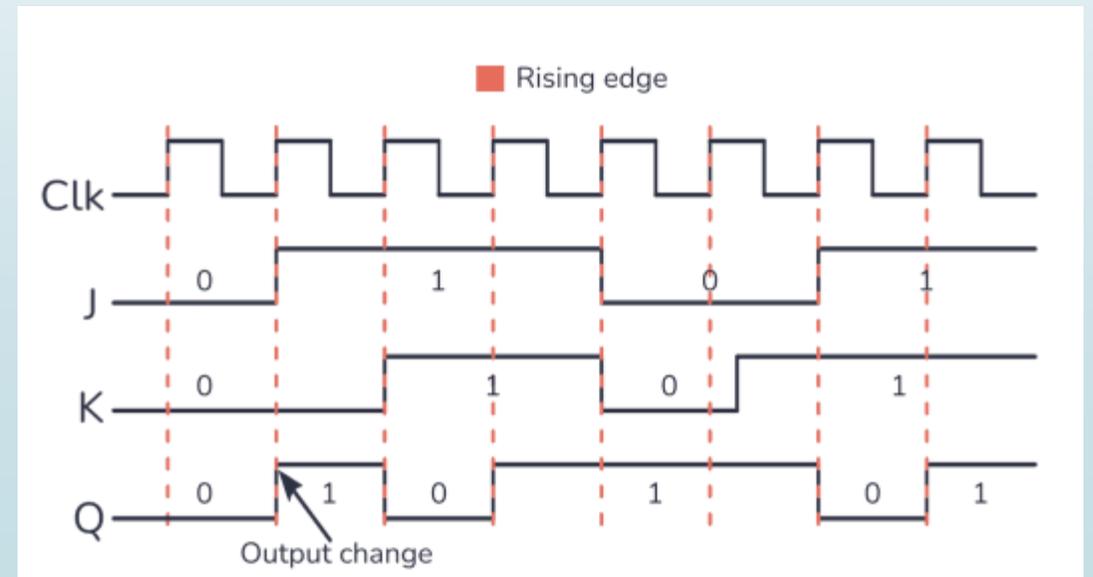
# The JK Flip-Flop

- ▶ The J and K inputs of the JK flip-flop can be used to set, reset, or toggle the output, like this:
- ▶  $J=0$  and  $K=0$ , the output Q (memory no change)
- ▶  $J=1$  and  $K=0$  sets the output to 1
- ▶  $J=0$  and  $K=1$  reset the output to 0
- ▶  $J=1$  and  $K=1$  toggle the output
- ▶ **But for the flip-flop to make any change, its Clock input must be 1.**



## Binary counter

- a **binary counter** is a type of **sequential logic circuit** which is able to count in binary numbers.
- The binary counters are built up of flip flops, where a flip flop is a most elementary memory element that can store 1-bit of information.
- In a binary counter, each flip flop represents one bit of the binary number. The counter increases its count by one whenever a clock pulse occurs.

# Applications of Binary Counters

- Binary counters are used in numerous digital systems.
- Binary counters are used in digital clocks and other digital timing devices.
- Binary counter can be used as a frequency divider, where it divides the frequency of the input signal by a fixed value.
- Binary counter can also be used as a shift register.
- In digital systems like computers, binary counters can be used as memory address decoders.
- Binary counter can also be used as a sequence generator, where it can generate sequences of binary codes.
- Binary counters can be used in error detection and correction applications.